

2012 01 - EE4313 Electronic Circuits II Exam #2

Part 1 (70 pts – includes take-home discussion)

Short Answer/Multiple Choice: (30 pts, 2 pts each)


Name:

Solutions

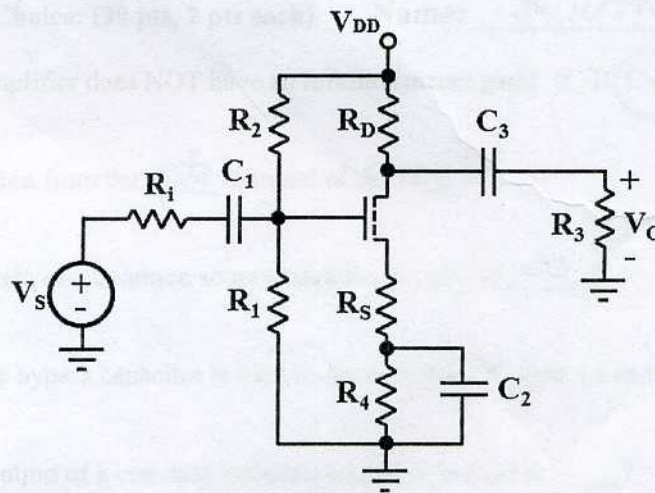1. Which type of FET amplifier does NOT have an infinite current gain? (C-D, C-G, C-S)
2. The output is never taken from the gate terminal of the FET.
3. The terminal current gain of a common source amplifier is typically ∞ ?
4. For a CE amplifier, the bypass capacitor is used to decrease the DC gain. (true, false)
5. The capacitor on the output of a common collector amplifier is used to ____? block DC from the load
6. When the gain of an amplifier is lowered, the input signal range (decreases, increases).
7. For calculating capacitor values for a specific frequency range, you should always use the (lower, upper) end of the range.
8. Conceptually, in order to act as a good coupling or bypass capacitor, the impedance of the capacitor must be much, much less than _____. resistance seen at its terminals
9. What is the advantage/disadvantage of only bypassing a part of the emitter resistance?
control gain vs. input signal range
10. What is the advantage of cascading multiple transistor amplifiers together?
obtain characteristics not possible with a single transistor
11. Why can r_o typically be neglected in our impedance calculations?
relatively large
12. $r_o = \beta (V_T / I_C)$ With all other parameters staying the same, how will removing R_E affect r_o ?
 I_C increases, $\therefore r_o$ decreases
13. How will bypassing R_E affect r_o ?
does not affect it
14. Is r_o affected at all by temperature? (Yes, No)
15. List two typical uses for the common collector amplifier.
impedance transformation
driver

Conceptual Amplifier Questions: (20 pts)

Given the diagram below, answer the following questions. You can express some answers in simple equation form such as $R_1 // R_1$ or $R_1 + R_2$, etcetera.



16. What type of amplifier is shown above?

C-S

17. For DC, what is the total resistance providing negative feedback.

$R_S + R_4$

18. How would you calculate the "rule-of-thumb" maximum value of I_{DS} ?

$$\frac{V_{DD}}{R_D + R_S + R_4}$$

19. If C_1 were removed, how would that complicate the design of this circuit?

the DC of the source would affect the bias point

20. If R_1 and R_2 were both reduced by a factor of 10 (ratio is unchanged), what would this affect?

power dissipation ~~and gain~~

21. How would removing R_D affect AC operation?

R_L & $R_{out} \rightarrow$ circuit would not work!

22. (4 pts) For AC operation, increasing R_S would accomplish two things, what are they?

reduce gain, increase input signal range

23. (4 pts) Write the equation(s) for DC power consumption.

$$P = \frac{V_{DD}^2}{R_1 + R_2} + (V_{DD} \times I_{DS})$$

24. BONUS: (5 pts) Suppose you determine a specific value of C_2 for a particular frequency range and the part is too expensive. You need to lower the required value of C_2 . What can you change in the circuit?

~~decrease~~ R_S & R_4


increase

2012 01 - EE4313 Electronic Circuits II Exam #2

Part 2 (65 pts)

Name: Solutions

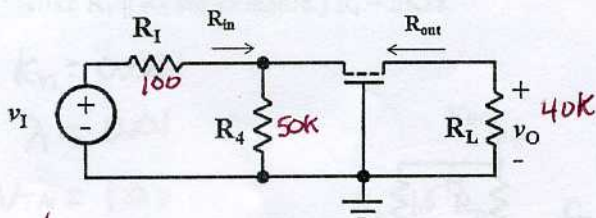1. (25 pts) What are the values for A_v , R_{in} , R_{out} , and A_i (i_o/i_i) for the amplifier shown below. $R_4 = 50k\Omega$, $R_I = 100\Omega$, and $R_L = 40k\Omega$. $V_{TN} = 0.8V$, $V_{GS} = 3V$, $V_{DS} = 5V$, $I_{DS} = 1mA$, and $\lambda = 0.005$.



$$g_m = \frac{2I_{DS}}{V_{GS} - V_{TN}} = \frac{2 \times 10^{-3}}{3 - 0.8} = 909 \mu S$$

$$r_o = \frac{1 + \lambda V_{DS}}{\lambda I_{DS}} = \frac{1.025}{5 \times 10^{-6}} = 205,000 \Omega$$

$$A_v = \left(\frac{g_m R_L}{1 + g_m R_{th}} \right) \cdot \left(\frac{50k}{50k + 100} \right) \quad R_{th} = R_4 \parallel R_I = 99.8 \Omega$$

$$= \frac{(909 \times 10^{-6})(40000)}{1 + (909 \times 10^{-6})(99.8)} \cdot (0.998) = 33.27$$

$$i_o = \frac{V_o}{R_L} \quad i_i = \frac{V_i}{R_I + R_4 \parallel R_{is}}$$

$$R_{in} = R_4 \parallel R_{is} \quad R_{is} = \frac{1}{g_m} = 1100 \Omega$$

$$A_i = \frac{V_o/R_L}{V_i/(R_I + R_{in})} = \frac{V_o}{V_i} \frac{(R_I + R_{in})}{R_L}$$

$$50000 \parallel 1100 = \frac{55 \times 10^6}{51,100} = 1076 \Omega$$

$$= 33.27 \frac{(100 + 1076)}{40000}$$

$$R_{out} = 205k [1 + (909 \times 10^{-6})(99.8)]$$

$$= 223.6k \Omega$$

$$= 0.978$$

$$A_i \approx +1$$

from formula sheet

2. (40 Total Points) Given the circuit and parameters below. BEFORE CALCULATING, MAKE SURE IT'S NOT ALREADY GIVEN!!!

For the common source amplifier: $V_{DD} = 10V$, $R_1 = 1\text{ M}\Omega$, $R_2 = 1.5\text{ M}\Omega$, $R_D = 5\text{ K}\Omega$, $R_S = 2\text{ K}\Omega$.
 $K_n = 0.01\text{ A/V}^2$, $\lambda = 0.01$, $V_{TN} = 1.0V$.

For the common collector amplifier: $R_4 = 60\text{ K}\Omega$, $R_3 = 40\text{ K}\Omega$, $R_C = 4\text{ K}\Omega$, $R_E = 300\text{ }\Omega$, $g_m = 0.4\text{ S}$, and $\beta_o = 100$. $R_5 = 1500\text{ }\Omega$.

(6 pts) Draw the AC equivalent circuit below this diagram. Calculate and show all equivalent resistances (like $R_1 \parallel R_2$ for example.) $R_1 = 5\text{ K}\Omega$.


$$k_n = 0.01$$

$$\lambda = 0.01$$

$$V_{TN} = 1.0V$$

$$g_m = 0.4$$


$$\beta = 100$$

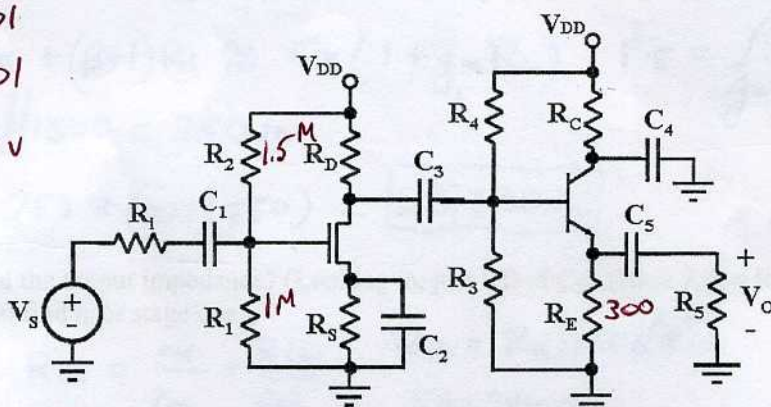


$$R_E \parallel R_5 = \frac{(300)(1500)}{1800} = 250\Omega$$

$$R_1 \parallel R_2 = \frac{(1.5\text{ M})(1\text{ M})}{2.5\text{ M}} = 600\text{ k}\Omega$$
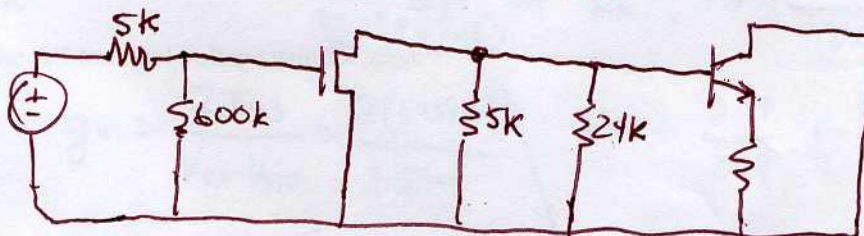
$$R_4 \parallel R_3 = \frac{(60\text{ K})(40\text{ K})}{100} = 24\text{ k}\Omega$$


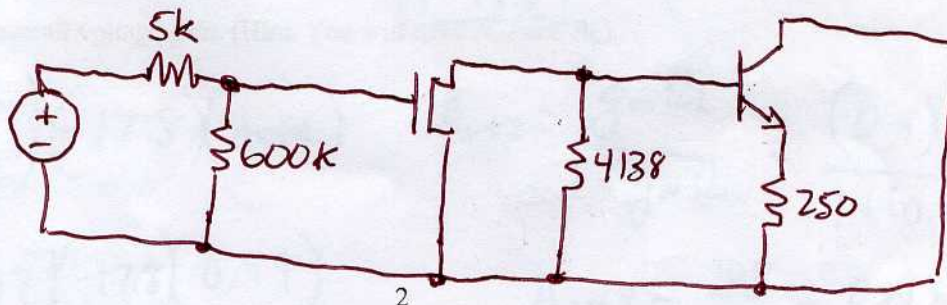
$$5\text{ k} \parallel 24\text{ k} = 4138$$



- a. (9 pts) For the DC operating point, write the 3 equations relating V_{GS} , V_{DS} , and I_{DS} . State any assumptions. Find V_{DS} and I_{DS} given $V_{GS} = 1.5V$. Neglect channel length modulation.

$$\textcircled{1} I_D = 7000 I_{DS} + V_{DS}$$

$$I_{DS} = 1.25 \text{ mA}$$

$$\textcircled{2} 4 = V_{GS} + 2000 I_{DS}$$

$$\textcircled{3} I_{DS} = \frac{K_n}{2} (V_{GS} - V_{TN})^2$$

$$I_D = 7000 I_{DS} + V_{DS}$$

$$V_{DS} = 1.25 \text{ V}$$

$$V_{EQ} = \left(\frac{1}{2.5}\right) 10 = 4V$$

- b. (5 pts) Find the terminal input impedance of stage 2 [R_{iB}]. (Looking in, just after R_3 and R_4).

$$R_{iB} = r_{\pi} + (\beta + 1) R_L \approx r_{\pi} (1 + g_m R_L) \quad r_{\pi} = \frac{\beta}{g_m} = \frac{100}{0.4} = 250 \Omega$$

$$R_L = 300 \parallel 1500 = 250 \Omega$$

$$R_{iB} = 250 + (101)(250) = 25,500 \Omega$$

- c. (5 pts) Find the output impedance? (Looking in, just left of C_5). (Hint: $R_{th} = R_D \parallel R_B \parallel R_{OUT}$ of stage 1 - you will need to find r_o of stage one.)

$$R_{OUT} = R_E \parallel R_{iE} \quad R_{iE} = \frac{\alpha}{g_m} + \frac{R_{th}}{\beta + 1}$$

$$R_E = 300 \Omega$$

$$\alpha = \frac{100}{101} = 0.990$$

$$g_m = 0.4 \text{ S} \quad \beta = 100$$

$$R_{th} = R_B \parallel 5k \parallel R_{iD}$$

$$R_B = 24k \Omega$$

$$R_{th} = 24k \parallel 5k \parallel 81k$$

$$= \frac{1}{\frac{1}{24k} + \frac{1}{5k} + \frac{1}{81k}} = 3937 \Omega$$

$$R_{iD} = r_o (1 + g_m R_s) \quad R_s = 0 \text{ bypassed}$$

$$r_o = \frac{1 + \lambda V_{DS}}{\lambda I_{DS}}$$

$$r_o = \frac{1 + (0.01)(1.25)}{(0.01)(1.25 \times 10^{-3})} = 81k \Omega$$

- d. (10 pts) Calculate the AC terminal voltage gain for stage 1.

$$A_{v1} = \frac{-g_m R_L}{1 + g_m R_s}$$

$$g_m = \frac{2I_{DS}}{V_{GS} - V_{TN}} = \frac{2(1.25 \times 10^{-3})}{1.5 - 1} = 5 \text{ mS}$$

$$R_{iE} = \frac{0.99}{0.4} + \frac{3937}{101} = 41.46 \Omega$$

$$R_{OUT} = 300 \parallel 41.46$$

$$= 36.4 \Omega$$

$$R_L = 5k \parallel 24k \parallel R_{iB}$$

$$= \frac{1}{\frac{1}{5k} + \frac{1}{24k} + \frac{1}{25520}} = 3560 \Omega \quad A_{v1} = \frac{(-5 \times 10^{-3}) R_L}{1} = -17.8$$

- e. (5 pts) Find the overall voltage gain. (Hint: You will need A_{v2} and R_L)

$$A_v = \left(\frac{600k}{605k}\right) (-17.8) (A_{v2})$$

$$A_{v2} = \frac{g_m R_L}{1 + g_m R_L} = \frac{(0.4)(250)}{1 + (0.4)(250)}$$

$$A_v = (0.9917)(-17.8)(0.99)$$

$$A_{v2} = \frac{100}{101} = 0.99$$

$$= -17.48$$

can approximate to one.